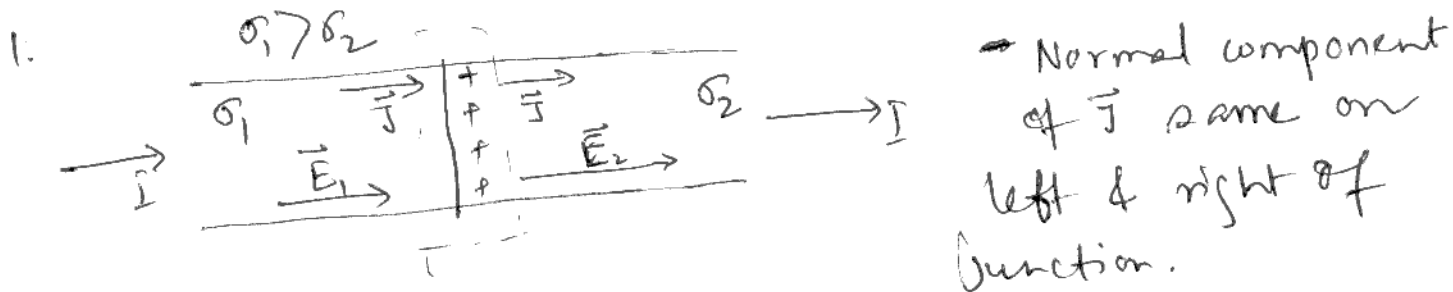


PHY102 : Quiz 1

1. A spherical charge distribution has a density ρ that is constant from $r = 0$ out to $r = R$ and is zero beyond. What is the electric field for all values of r , both less than and greater than R ? [2.5]

Assignment 5 (Sols.)



$$\therefore |\vec{E}_1| = \frac{J}{\sigma_1} \quad , \quad |\vec{E}_2| = \frac{J}{\sigma_2} \quad (\because \sigma_1 > \sigma_2 \therefore E_2 > E_1)$$

By Gauss's law, the difference in the electric fields gives the surface charge density, σ' as,

$$E_2 - E_1 = \frac{\sigma'}{\epsilon_0}$$

$$\Rightarrow \frac{J}{\sigma_2} - \frac{J}{\sigma_1} = \frac{\sigma'}{\epsilon_0} \Rightarrow \sigma' = \frac{J\epsilon_0}{\sigma_2} \left(\frac{1}{\sigma_2} - \frac{1}{\sigma_1} \right)$$

If A is the area of the interface, then,

$$Q = \sigma' A \quad \& \quad I = JA = \frac{JQ}{\sigma'}$$

$$\therefore Q = \frac{I\sigma'}{J} = \frac{I}{J} \cdot \frac{J\epsilon_0}{\sigma_2} \left(\frac{1}{\sigma_2} - \frac{1}{\sigma_1} \right)$$

$$\therefore \boxed{Q = \frac{I\epsilon_0}{\sigma_2} \left(\frac{1}{\sigma_2} - \frac{1}{\sigma_1} \right)}$$

2. Designate the corners of a square, l on a side, in clockwise order, A, B, C, D . Put charges $2q$ at A and $-3q$ at B . Determine the value of the line integral of \mathbf{E} , from point C to point D . (No actual integration needed!) What is the numerical answer if $q = 10^{-9} \text{C}$ and $l = 5 \text{cm}$? [2.5]

$$2. \quad I = \frac{V}{R} = V \cdot \left(\frac{A}{\rho L} \right) \quad (\because R = \frac{\rho L}{A}, \rho: \text{resistivity})$$

$$J = \frac{I}{A} = \frac{VA/\rho L}{A} = \frac{V}{\rho L}$$

Now, $J = ne v_d$ where n : no. of electrons
 cm^3

v_d : drift velocity of electron.

$$\therefore ne v_d = \frac{V}{\rho L} \Rightarrow v_d = \frac{V}{\rho L n e}$$


$$\rho = 1.7 \times 10^{-6} \text{ ohm cm}, \quad n = 8 \times 10^{22} / \text{cm}^3$$

$$e = 1.6 \times 10^{-19} \text{ C}, \quad V = 6 \text{ volt}, \quad L = 1 \text{ km} = 10^5 \text{ cm.}$$

$$\therefore v_d \approx 2.8 \times 10^{-3} \text{ cm/s.}$$

$$\therefore t \approx \frac{10^5 \text{ cm}}{2.8 \times 10^{-3} \text{ cm/s}} \approx 3.6 \times 10^7 \text{ s} \approx 1 \text{ yr} !$$

3.

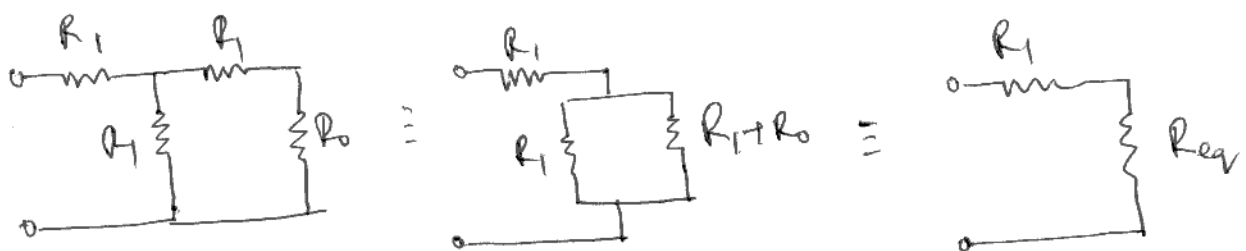

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_1 + R_0}} = \frac{R_1 (R_1 + R_0)}{R_1 + (R_1 + R_0)}$$

$$\text{Finally, } R = R_1 + R_{eq} = R_1 + \frac{R_1 (R_1 + R_0)}{R_1 + R_1 + R_0}$$

We require, $R = R_0$.

PHY102 : Quiz 1

1. A spherical charge distribution has a density ρ that is constant from $r = 0$ out to $r = R$ and is zero beyond. What is the electric field for all values of r , both less than and greater than R ? [2.5]



$$\therefore R_0 = R_1 + \frac{R_1(R_1 + R_0)}{2R_1 + R_0} \Rightarrow \frac{R_1(2R_1 + R_0) + R_1(R_1 + R_0)}{2R_1 + R_0}$$

$$\Rightarrow R_0(2R_1 + R_0) = R_1(2R_1 + R_0 + R_1 + R_0) = R_1(3R_1 + 2R_0)$$

$$\Rightarrow 2R_0R_1 + R_0^2 = 3R_1^2 + 2R_0R_1 \Rightarrow R_0^2 = 3R_1^2$$

$$\therefore \boxed{R_1 = \frac{R_0}{\sqrt{3}}}$$

4.

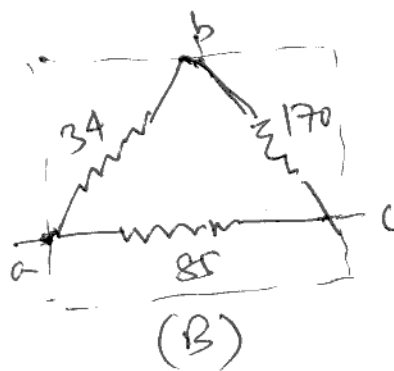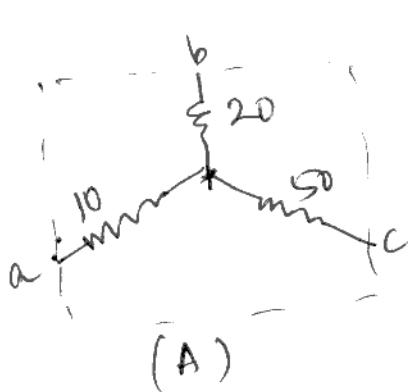

For (A), resistance between any 2 terminals is basically the series combo of the 2 resistors which connect the terminals. The third resistance does not feature. Therefore, the resistance between terminals (a) & (b) would be,

$$R_{ab}^A = (10 + 20) \Omega = 30 \Omega.$$

For (B), resistance between 2 terminals would involve a resistor in \parallel with 2 others being in series. For example, to find the resistance between terminals (a) & (b), 34Ω is in \parallel to the

2. Designate the corners of a square, l on a side, in clockwise order, A, B, C, D . Put charges $2q$ at A and $-3q$ at B . Determine the value of the line integral of \mathbf{E} , from point C to point D . (No actual integration needed!) What is the numerical answer if $q = 10^{-9}C$ and $l = 5cm$? [2.5]

series combination of 170Ω and 85Ω .


$$\therefore R_{AB} = \left(\frac{1}{\frac{1}{34} + \frac{1}{170+85}} \right) \Omega = \frac{1}{\frac{255+34}{34 \times 255}}$$

$$= \frac{15 \times 255 \times 34}{289} = 30\Omega = R_{AB}^A$$

You can similarly show for the other 2.

These are the only 2 possible configurations.

5.

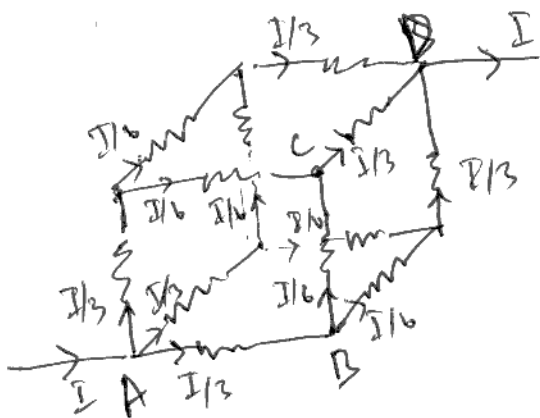

Resistors at the edges of the cube all have same value R_0 . A current I entering at A will get equally divided in the three sides and so on.


Now take any path say $ABCD$ & for that path,

$$V_{AD} = \underbrace{\frac{I}{3} R_0}_{AB} + \underbrace{\frac{I}{6} R_0}_{BC} + \underbrace{\frac{I}{3} R_0}_{CD} = \frac{5}{6} R_0 I$$

$$\therefore R_{AD} = \frac{V_{AD}}{I} = \frac{5}{6} R_0$$

PHY102 : Quiz 1

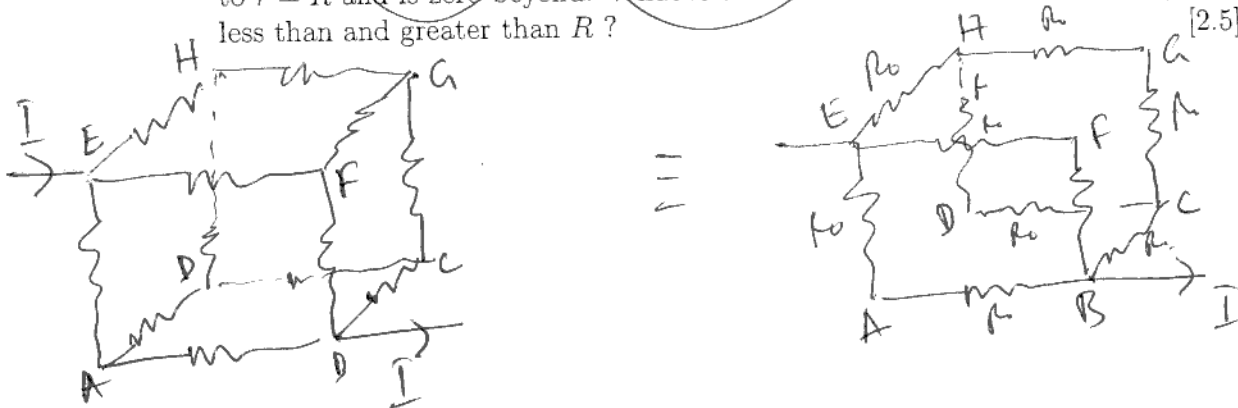1. A spherical charge distribution has a density ρ that is constant from $r = 0$ out to $r = R$ and is zero beyond. What is the electric field for all values of r , both less than and greater than R ? [2.5]




By symmetry, A & F & D & C are equivalent. Current in the branches AD & FC must be zero.




$$\frac{1}{R_{eq}} = \frac{1}{R_0 + R_0} + \frac{1}{R_0 + R_0} = \frac{1}{R_0}$$

$$\therefore R_{eq} = R_0$$

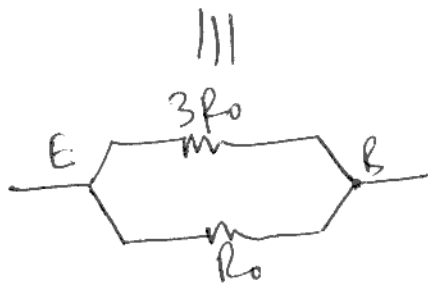
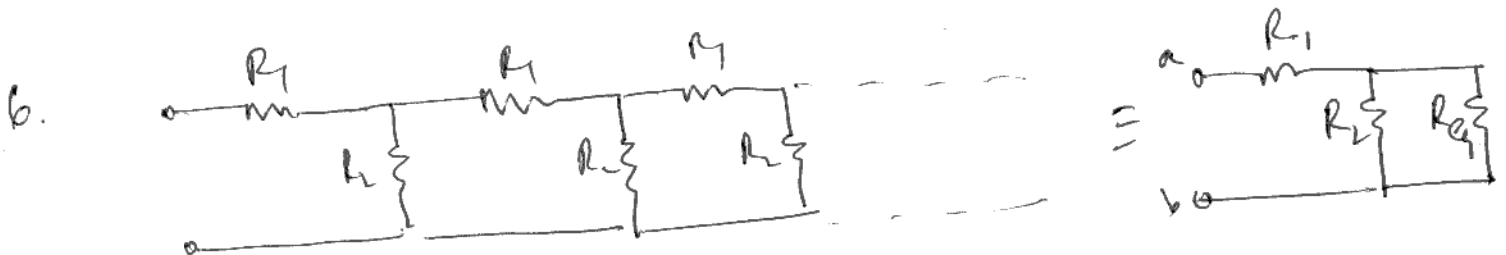
$$R_{EB} = \frac{1}{\frac{1}{3R_0} + \frac{1}{R_0}} = \frac{3}{4} R_0$$



Let R_{eq} be the equivalent resistance. For the infinite ch, we can replace everything on the right of the first 2 elements by R_{eq} . ~~and still get the equation~~


$$\text{But, } R_{ab} = R_{eq} \quad \therefore R_{eq} = R_1 + \frac{R_{eq} \cdot R_2}{R_{eq} + R_2}$$

2. Designate the corners of a square, l on a side, in clockwise order, A, B, C, D . Put charges $2q$ at A and $-3q$ at B . Determine the value of the line integral of \mathbf{E} , from point C to point D . (No actual integration needed.) What is the numerical answer if $q = 10^{-9}C$ and $l = 5cm$? [2.5]

$$k_{eq} + k_{eq}R_2 = k_{eq}R_1 + I_1R_2 + k_{eq}R_2$$

$$\Rightarrow k_{eq} - k_{eq}R_1 - I_1R_2 = 0$$
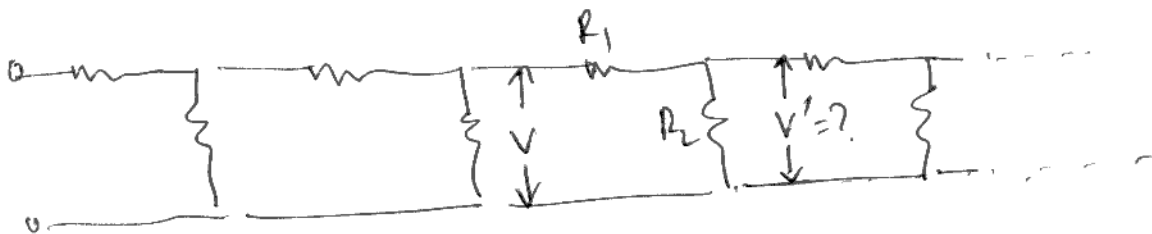
$$k_{eq} = \frac{R_1 + \sqrt{R_1^2 + 4I_1R_2}}{2} \quad (\text{NOT the -ve root why?})$$



Consider the loop region

$$V' = I_2 R_{eq} \quad \& \quad I_2 R_{eq} - I_1 R_2 = 0$$


$$\therefore V' = I_1 R_2$$

$$\text{Also, } V = I R_1 + I_1 R_2 = I R_1 + V'$$

$$\Rightarrow V' = V - I R_1$$

But, $V = I R_{eq}$. since equivalent resistance between pts a & b is still R_{eq} .
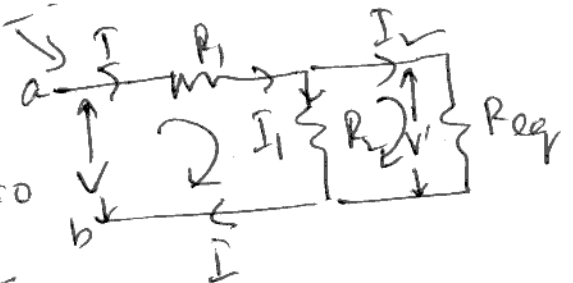
$$\therefore V' = V - \frac{V R_1}{R_{eq}} = V \left(\frac{R_{eq} - R_1}{R_{eq}} \right)$$



2. Designate the corners of a square, l on a side, in clockwise order, A, B, C, D . Put charges $2q$ at A and $-3q$ at B . Determine the value of the line integral of E , from point C to point D . (No actual integration needed!) What is the numerical answer if $q = 10^{-9}C$ and $l = 5cm$? [2.5]

$$q \quad \frac{V'}{V} = \frac{1}{2} \Rightarrow \frac{1}{2} = \frac{R_{eq} - R_1}{R_{eq}} \Rightarrow R_{eq} = 2R_{eq} - 2R_1$$

$$\therefore R_{eq} = 2R_1.$$

$$\text{Now, } R_{eq} = R_1 + \sqrt{R_1^2 + 4R_1R_2}$$

$$\therefore R_1 + \sqrt{R_1^2 + 4R_1R_2} = 2R_1 \Rightarrow R_1^2 + 4R_1R_2 = R_1^2$$

$$\Rightarrow 2R_1^2 = 4R_1R_2 \Rightarrow \boxed{R_2 = 2R_1}.$$

To terminate ladder, just ~~connect~~ replace rest of ladder at any pt by the equivalent resistance R_{eq} .